


SN74HC595 drives 4-digit digital tube Experiment

74HC595 Introduction

The 74HC595 is a CMOS shift register containing 8-bit serial input and parallel open-drain output that provides data to a register with three-state output. Shift register and storage register, respectively, have an independent clock respectively, the shift register 74 hc595 are needed with the highest priority (SRCLR) directly in the end, serial input (DS) used to cascade of serial output at the next higher level, when the output enable (OE) is a high end, 74 hc595 are needed in parallel in a high impedance state, output for the low level is enabled for parallel output.

Both the shift register clock SHCP and the storage register clock STCP are raised edge triggers.

Pinning information

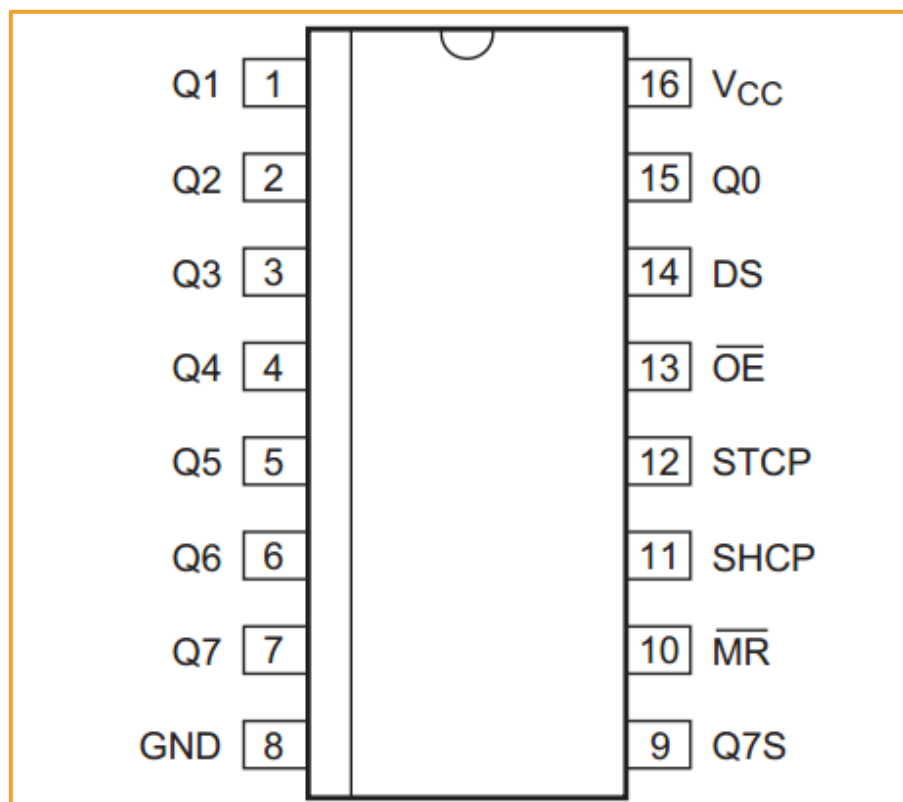

Pin description

Symbol	Pin	Description
Q0	15	parallel data output 0
Q1	1	parallel data output 1
Q2	2	parallel data output 2
Q3	3	parallel data output 3
Q4	4	parallel data output 4
Q5	5	parallel data output 5
Q6	6	parallel data output 6
Q7	7	parallel data output 7
GND	8	ground(0V)
Q7S	9	serial data output
MR	10	master reset(active low)
SHCP	11	shift register clock input
STCP	12	storage register clock input
OE	13	output enable input(active low)
DS	14	serial data input
Vcc	16	supply voltage


Experiment Purpose

In this experiment, we used Arduino to drive the serial output to 74HC595, and then the parallel port of 74HC595 to drive a common cathode four-digit digital tube. Then driven directly by the Arduino digital tube of a foot, this experiment using eight 220 Ω resistance limit current role, let the dynamic display of digital tube digital has been reduced to 0 from 9.

Component List

- ◆ Keywish Arduino UNO R3 mainboard
- ◆ 4-7Segment cathode tube * 1
- ◆ SN74HC595 * 1
- ◆ 220 Ω resistor* 8
- ◆ Several jumper wires

Schematic Diagram

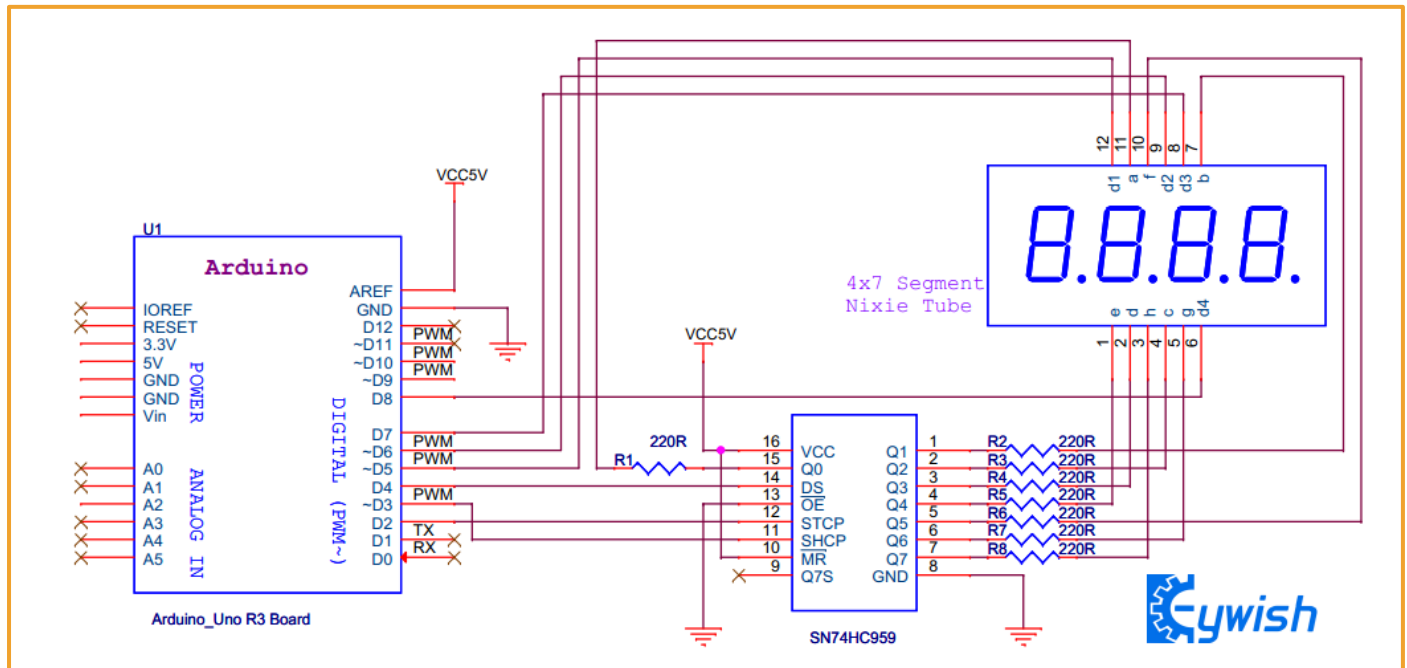

Wiring of Circuit

arduino Uno	SN74HC595
2	12(STCP)
3	11(SHCP)
4	14(DS)

arduino Uno	7 Segment nixie tube
5	12
6	9
7	8
8	6


SN74HC595	7 Segment nixie tube
15	11
1	7
2	5
3	2
4	1
5	10
6	5
7	3

Code

```
#define BIT_CHOICE_1  5
#define BIT_CHOICE_2  6
#define BIT_CHOICE_3  7
#define BIT_CHOICE_4  8
#define STCP_PIN  2
#define SHCP_PIN  3
#define DATA_PIN  4 //define stcp shcp ds pin
int BIT_CHOICE[4]= {BIT_CHOICE_1 ,
BIT_CHOICE_2 ,BIT_CHOICE_3,BIT_CHOICE_4};// 4x8bit
unsigned char
DisplayNumble[10]={0x00,0x6F,0x7F,0x07,0x7D,0x6D,0x66,0x4F,0x5B,0X06};
void setup()
{
    pinMode(STCP_PIN,OUTPUT);
    pinMode(SHCP_PIN,OUTPUT);
    pinMode(DATA_PIN,OUTPUT); //set stcp shcp ds pin putput mode
    for(int i=0;i<4;i++)
    {
        pinMode(BIT_CHOICE[i],OUTPUT);
        digitalWrite(BIT_CHOICE[i],HIGH);
    }
}
void nixie_pin_chioce_set(int value)
{
    for(int i=0;i<4;i++)
    {
        digitalWrite(BIT_CHOICE[i],value);
    }
}
```

```
void loop()
{
    int i=0;
    for(i = 9; i>=0 ;i-- )    // numble 9 - > 0 down
    {
        nixie_pin_chioce_set(HIGH);
        digitalWrite(STCP_PIN,LOW);
        shiftOut(DATA_PIN,SHCP_PIN,MSBFIRST,DisplayNumble[i]); //serial
        shift out put display numble
        digitalWrite(STCP_PIN,HIGH);
        nixie_pin_chioce_set(LOW);
        delay(1000);
    }
}
```

Experiment Result

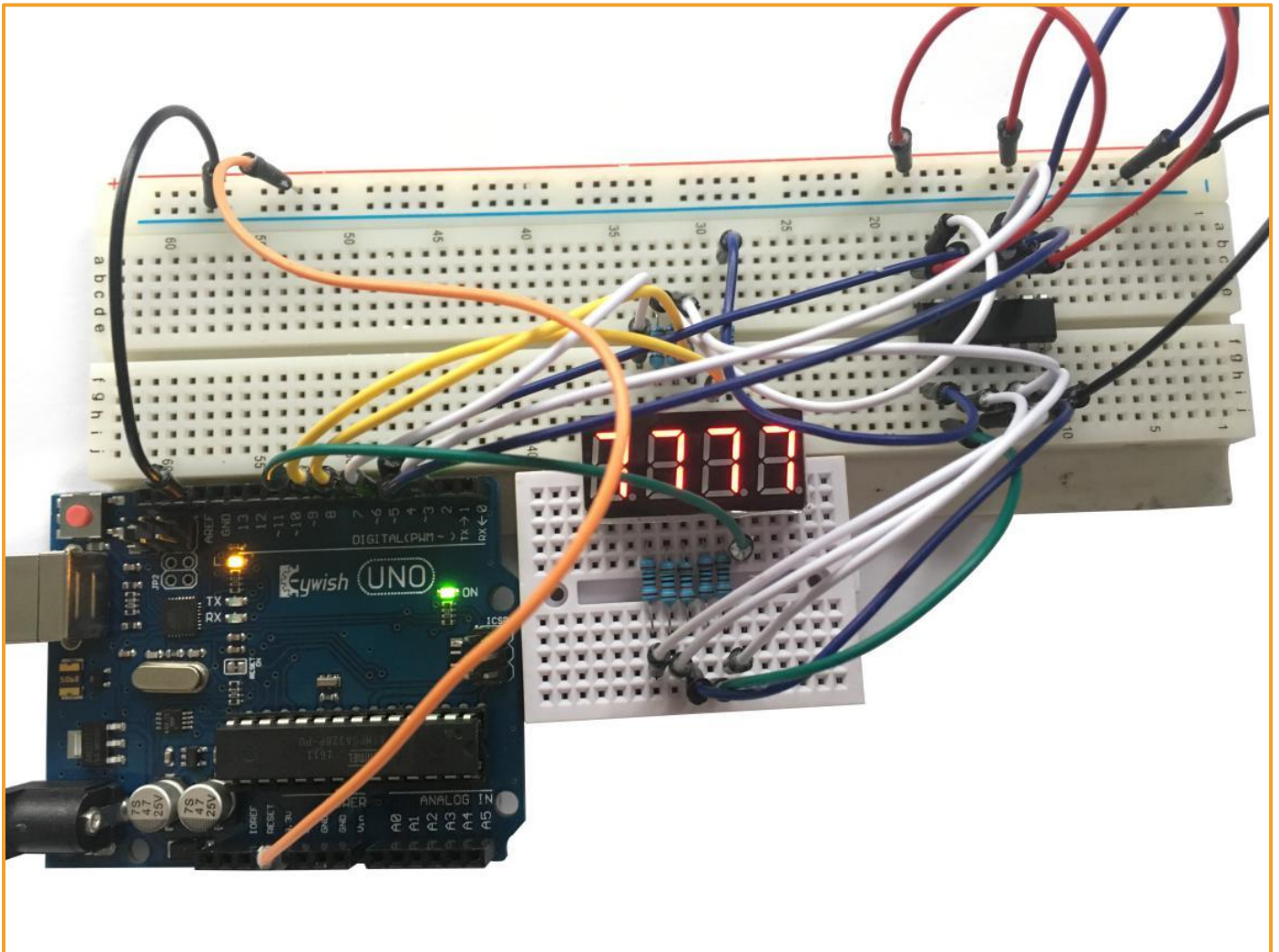

Mixly programming program

```

74HC595 digital tube initialization BIT_CHOICE_1 5 BIT_CHOICE_2 6 BIT_CHOICE_3 7 BIT_CHOICE_4 8 STCP_PIN 2 SHCP_PIN 3 DATA_PIN 4
Declare ShowTime as int value 60
Declare NowTime as long value 0
Declare oldTime as long value 1

setup
  74HC595 digital tube off

NowTime = System running time ms + 1000
if NowTime == oldTime
do
  oldTime = oldTime + 1
  ShowTime = ShowTime - 1
74HC595 digital tube display
if ShowTime == 0
do repeat while true
do 74HC595 digital tube off

```

Magicblock graphical programming program

